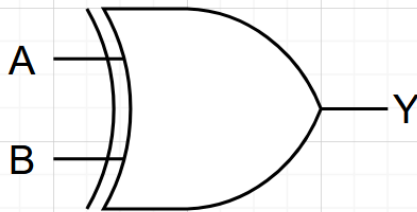


CS4093 - Assignment 1

Alexander Stradnic - 119377263

XOR : An Exclusive OR gate works in a similar manner to OR, except that it only activates on one of the inputs only, not both.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0



Verilog Code

```
module xor_gate (c,a,b);
    input    a,b;
    output   c;
    assign c = a^b;
endmodule
```

Testbench Code

```
module xorgate;
    reg a;
    reg b;
    wire c;

    xor_gate TEST(.c(c), .a(a), .b(b));

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
        a=0;
        b=0;
        #10;
        a=0;
        b=1;
        #10;
    end
endmodule
```


```

    a=1;
    b=0;
    #10;
    a=1;
    b=1;
    #10;

end
endmodule


```

Waveform

 

NAND : A NAND gate works by inverting the output taken from an AND gate.

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

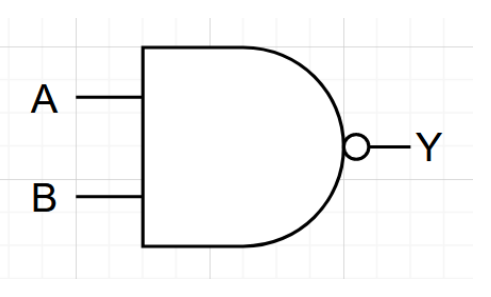

Verilog Code

```

module nand_gate (c,a,b);
    input    a,b;
    output   c;
    assign c = !(a&b);
endmodule

```

Testbench Code:

```

module nandgate;
    reg a;
    reg b;
    wire c;

    nand_gate TEST(.c(c), .a(a), .b(b));

    initial begin


```

```

    $dumpfile("dump.vcd");
    $dumpvars(1);
    a=0;
    b=0;
    #10;
    a=0;
    b=1;
    #10;
    a=1;
    b=0;
    #10;
    a=1;
    b=1;
    #10;
end
endmodule


```

Waveform

 

NOR : A NOR gate works by inverting the output from an OR gate.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

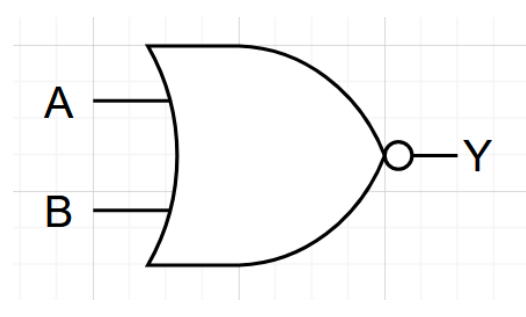

Verilog Code

```

module nor_gate (c,a,b);
    input    a,b;
    output   c;
    assign c = !(a|b);
endmodule

```

Testbench Code

```

module norgate;

```


```
reg a;  
reg b;  
wire c;  
  
nor_gate TEST(.c(c), .a(a), .b(b));  
  
initial begin  
    $dumpfile("dump.vcd");  
    $dumpvars(1);  
    a=0;  
    b=0;  
    #10;  
    a=0;  
    b=1;  
    #10;  
    a=1;  
    b=0;  
    #10;  
    a=1;  
    b=1;  
    #10;  
end  
endmodule
```

Waveform



SR FLIP FLOP : An SR flip-flop can store a 1-bit value, and operates using 2 NAND gates. An input is designated as the setter (S) with the other input being the resetter (R).

S	R	Q	Q'	State
0	0	Q	Q'	No change
1	0	1	0	Set
0	1	0	1	Clear
1	1	X	X	Invalid

 

Verilog Code

```

module sr_flipflop(q,qbar,clk,s,r);
input clk;
input s;
input r;
output q,qbar;
reg q,qbar;
always @(posedge clk) begin
    if (r == 0 && s==0) begin
        q <= q;
        qbar <= qbar;
    end else if (s == 1 && r == 0) begin
        q <= 1;
        qbar <= 0;
    end else if (s == 1 && r == 1) begin
        q <= 1'bx;
    end
end

```

```

qbar <= 1'bx;
end else if (s == 0 && r == 1) begin
q <= 0;
qbar <= 1;
end
end
endmodule

```

Testbench Code

```

module TEST;
reg clk,s,r;
wire q,qbar;
sr_flipflop TEST (.q(q), .qbar(qbar), .clk(clk), .s(s),.r(r));
initial begin
$dumppfile("dump.vcd");
$dumppvars(1);
clk=1; // initial
r = 0;
s = 0;
#10;
clk=0; // set but clock inactive
r = 0;
s = 1;
#10;
clk=1; // clock active, thus set works
#10;
clk=0; // reset but clock inactive
r = 1;
s = 0;
#10;
clk = 1; // reset activates
#10;
clk = 0;
s = 1; // bad state but not active
#10;
clk = 1; // bad state activated
#10;
end
endmodule


```

Waveform



JK FLIP FLOP : A JK flip-flop can store a 1-bit value, and operates using 2 NAND gates, in a similar manner to the SR flip-flop. The JK Flip-flop overcomes the issue with the SR flip-flop where the state is invalid when both inputs are set to 1 by flipping the state of the outputs in that instance.

J	K	Q	Q'	State
0	0	Q	Q'	No change
1	0	1	0	Set
0	1	0	1	Clear
1	1	$\sim Q$	$\sim Q'$	Toggle State

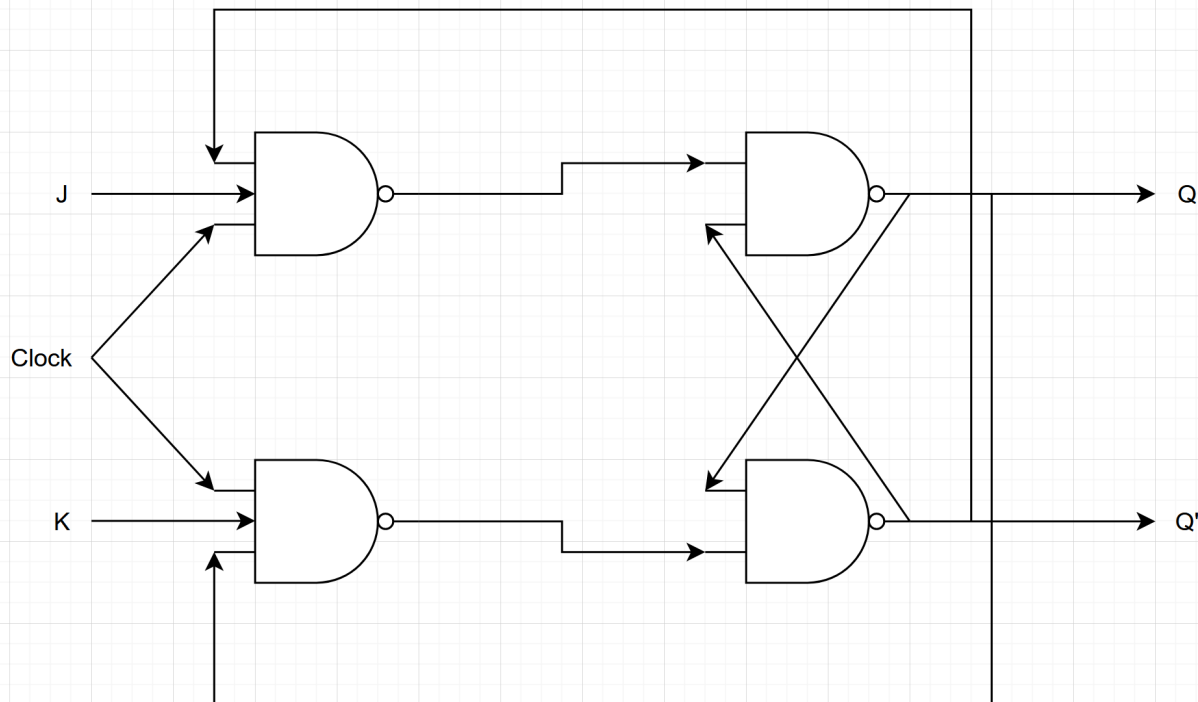

Verilog Code

```

module jk_flipflop(q,qbar,clk,j,k);
input clk;
input j;
input k;
output q,qbar;
reg q,qbar;
always @(posedge clk) begin
    if (j==0 && k==0) begin

```

```

q <= ~q;
qbar <= ~qbar;
    end else if (j == 1 && k == 0) begin
q <= 1;
qbar <= 0;
    end else if (j == 1 && k == 1) begin
q <= ~q;
qbar <= ~qbar;
    end else if (j == 0 && k == 1) begin
q <= 0;
qbar <= 1;
end
end
endmodule

```

Testbench Code

```

module TEST;
reg clk,j,k;
wire q,qbar;
    jk_flipflop TEST (.q(q), .qbar(qbar), .clk(clk), .j(j),.k(k));
initial begin
$dumpfile("dump.vcd");
$dumpvars(1);
clk=1; // initial
j = 0;
k = 0;
#10;
clk=0; // set but clock inactive
j = 0;
k = 1;
#10;
clk=1; // clock active, thus set works
#10;
clk=0; // reset but clock inactive
j = 1;
k = 0;
#10;
clk = 1; // reset activates
#10;
clk = 0;
k = 1; // bad state but not active

```




```
#10;  
clk = 1; // bad state activated  
#10;  
end  
endmodule
```

Waveform



T FLIP FLOP : An T flip-flop can store a 1-bit value, and flips with the input (AND clock if relevant).

T	Q	Q'	State
0	Q	Q'	Hold State
1	$\sim Q$	$\sim Q'$	Toggle State

 

Verilog Code

```
module t_flipflop(q,qbar,clk,t);
input clk;
input t;
output q,qbar;
reg q,qbar;

always @(posedge clk) begin
    if(q === 1'bx) begin
        q <= 1;
        qbar <= 0;
    end else if (t == 0) begin
        q <= q;
        qbar <= qbar;
    end else if (t == 1) begin
        q <= ~q;
        qbar <= ~qbar;
    end
end
```

```
end
endmodule
```

Testbench Code

```
module TEST;
  reg clk,t;
  wire q,qbar;
  t_flipflop TEST (.q(q), .qbar(qbar), .clk(clk), .t(t));
  initial begin
    $dumpfile("dump.vcd");
    $dumpvars(1);
    clk=1; // initial
    t = 0;
    #10;
    clk=0; // toggle but clock inactive
    t = 1;
    #10;
    clk=1; // clock active, thus toggle works
    #10;
    clk=0; // hold but clock inactive
    t = 0;
    #10;
    clk = 1; // hold 'activates'
    #10;
    clk = 0;
    t = 1; // toggle but not active
    #10;
    clk = 1; // toggle state activated
    #10;
  end
endmodule
```

Waveform

